
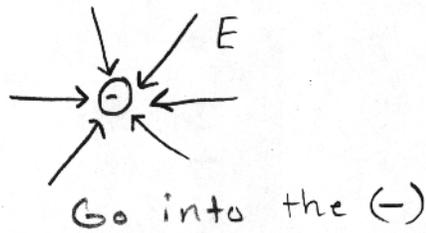


Intro. to Circuits

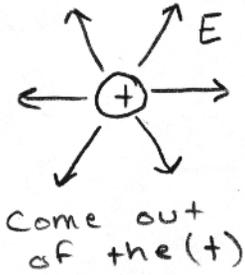- Charges create electric fields. (E)
 - Can be represented as field lines.




- These fields represent the force a charge would experience if it was in the E -field.

These E -fields can form inside wires when a potential difference is applied.


What is this?

Analogy to height in a gravity field!

$$W = F \cdot d = -\Delta U_g$$

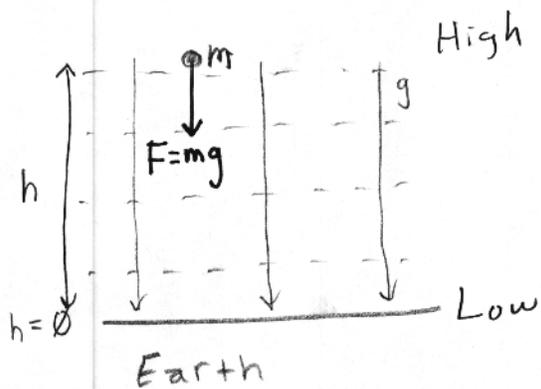

$$U_g = mgh$$

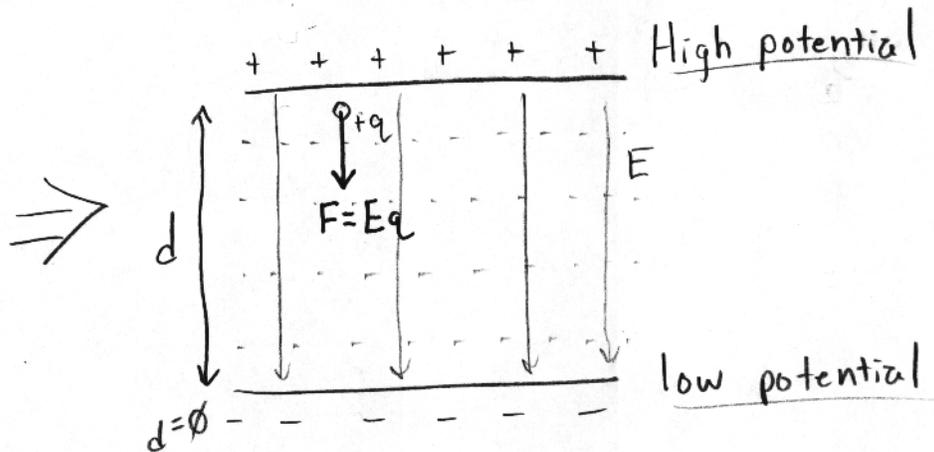

$$U_e = Eqd$$

$$\Delta V = E \cdot d$$

ΔV = potential difference
also called voltage!


(ΔV) potential difference is provided by a voltage source. (batteries, generators, cells)

The potential difference causes an EMF, electromotive force, which drives the flow of charge.

EMF - is not really a force, it's the work done per unit charge.

Electric Current

wire

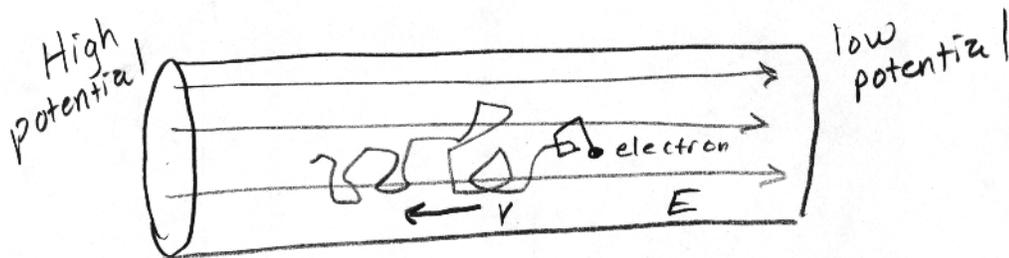

When a potential difference is applied to a conductive wire, an E-field forms inside at the speed of light.

- The charges (electrons) do not move this fast.
- They simply have a net movement through the E-field.

Current

- The amount of charge passing a cross-sectional area in a given amount of time.

$$\boxed{I_{\text{avg}} = \frac{\Delta Q}{\Delta t}}$$

current

units


$$\frac{C}{s} = \text{Ampere (Amps)}$$


- So why do we say current flows from positive (high V) to negative terminals (low V) of a battery?
- Electrons really go from (low V) to (high V)
- However, conventional current, was established prior to the discovery of electrons!

★ We will use conventional current

- Current (I) will flow from (+) high to (-) low

Current is like flowing water.

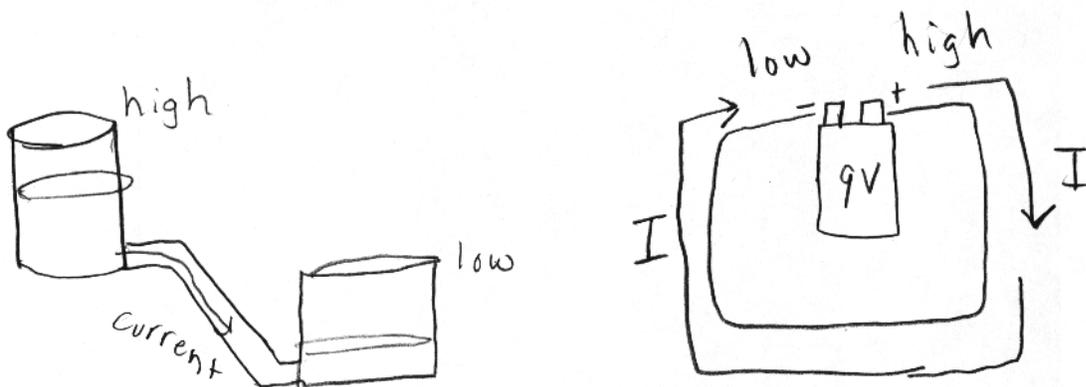

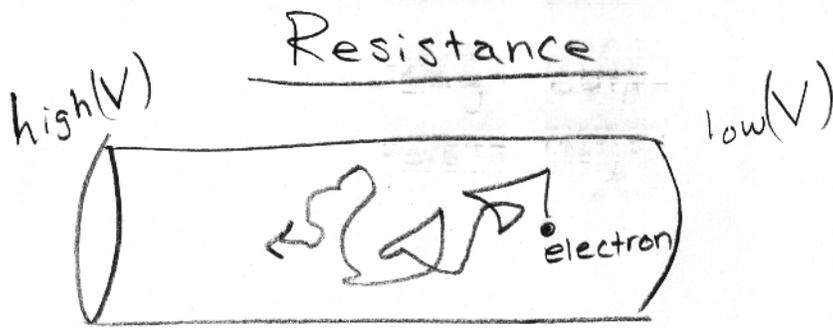

Why does the electron move so erratically?


All material have some resistance. It is determined by the wire.

$$R = \frac{\rho l}{A}$$

ρ = resistivity constant (varies based on material)

l = length

A = cross-sectional area

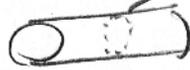

$$A = \pi r^2$$

• units of resistance are based on Ohm's Law


Ohm's Law

$$I = \frac{\Delta V}{R}$$

unit for resistance

$$R = \frac{\Delta V}{I} = \frac{\text{Volts}}{A} = \Omega \text{ (ohm's)}$$

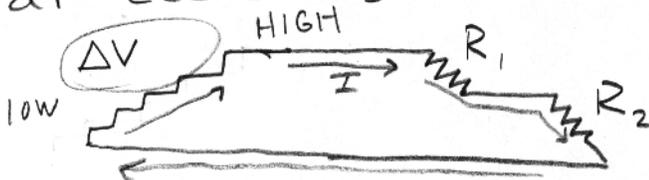★ Resistors are appliances that often do work.
 • When work is done by the resistor the potential decreases.



Power and Energy

• Many electrical devices are rated by the amount of power they use.

Power (Watts)

$$P = I \Delta V = \text{Amps} \cdot \text{Volts} = \text{Watts}$$

Apply Ohm's law to derive...

$$P = \left(\frac{\Delta V}{R} \right) \Delta V = \frac{\Delta V^2}{R} \quad I = \frac{\Delta V}{R}$$

$$P = I \cdot (I R) = I^2 R \quad \Delta V = I \cdot R$$

3 ways to find Power

$$P = I \Delta V = \frac{\Delta V^2}{R} = I^2 R$$

★ Energy dissipated by appliance

$$P = \frac{W}{t}$$

W = Energy in action

$$P = \frac{E}{t}$$

$$E = P_t = I \Delta V \cdot t$$


Circuit Analysis

• We use circuit analysis to find information about a circuit's components.


Ohm's Law is our key


$$I = \frac{\Delta V}{R}$$

Schematic symbols for circuits

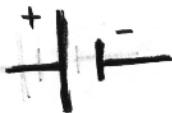
Battery 

Resistor  • Lightbulb 

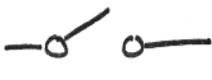Switch 

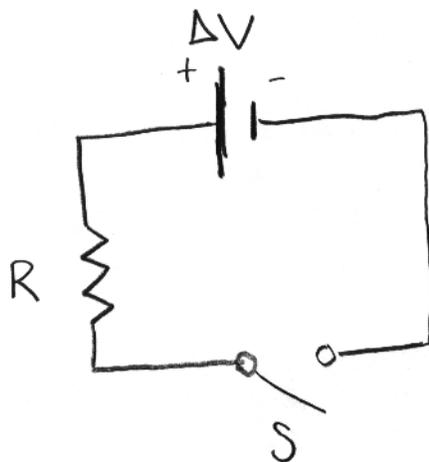

Basic circuit

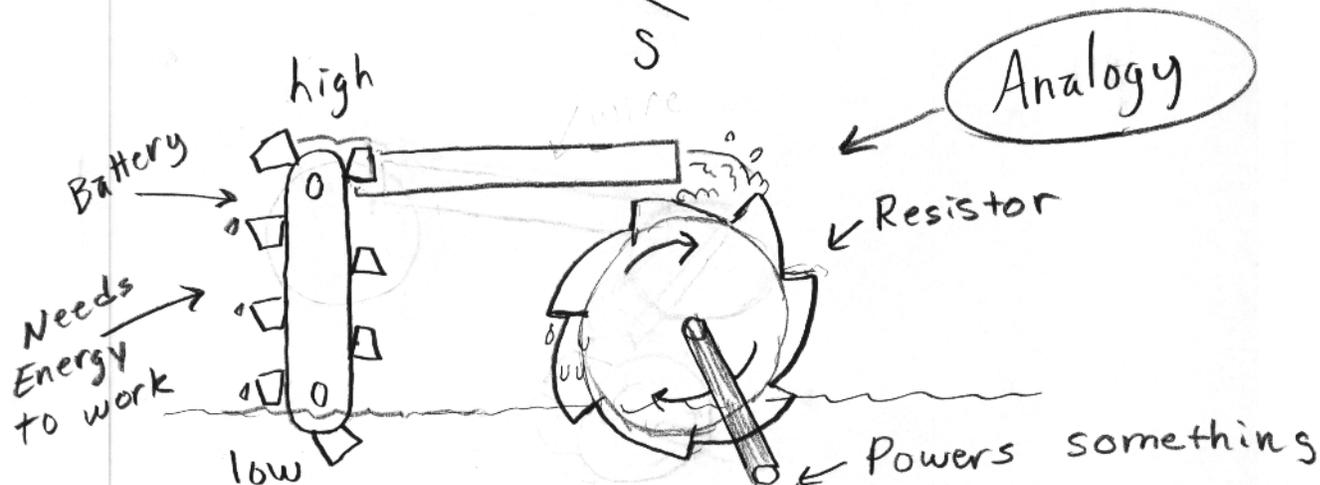


Combining Resistors

2 ways to combine

Series



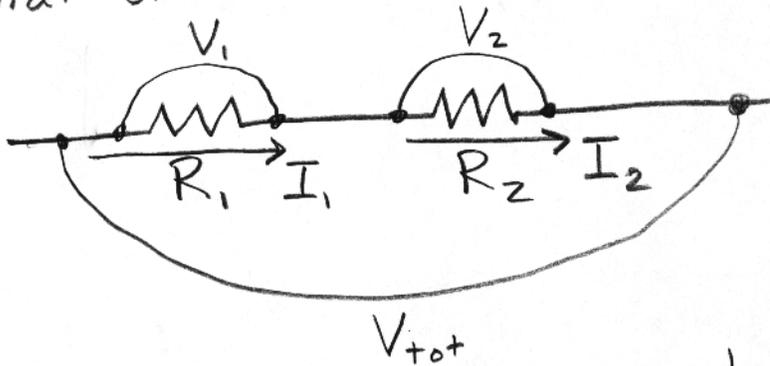- wired one after another
- Same current must go through every resistor
- Potential difference is different across each resistor



$$I_1 = I_2$$


$$V_1 + V_2 = V_{tot}$$

- The combined resistance, equivalent resistance, is...

$$R_{eq} = R_1 + R_2 \dots$$


$$R_{eq} = \sum R_i$$

Parallel

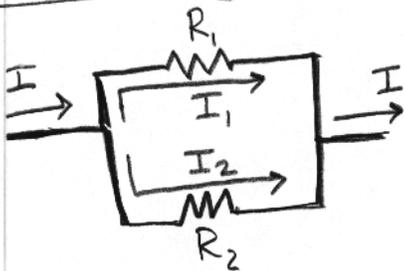

- wired on different paths
- current is different across each resistor
- Potential difference is same across both resistors

Parallel V

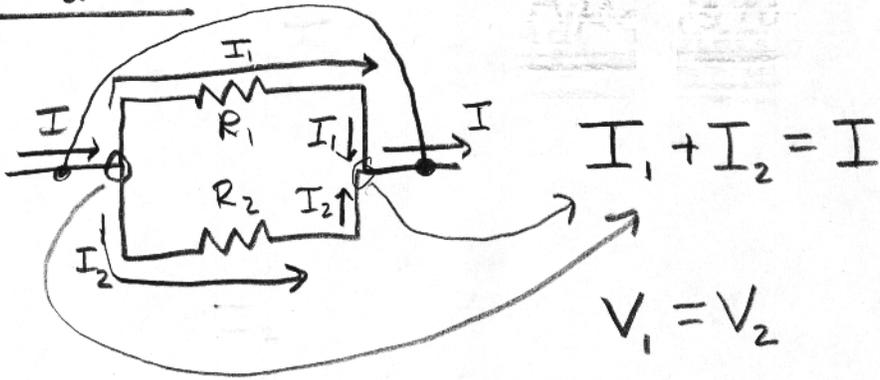


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \dots$$

$$\frac{1}{R_{eq}} = \sum \frac{1}{R_i}$$

So lets use this.

Ex 1:

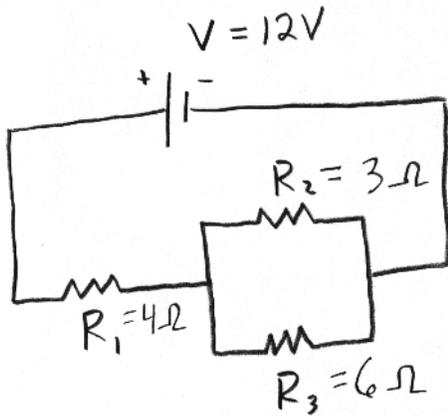


a) Find equivalent resistance of circuit.

- First, find R_{eq} of the resistors in parallel

$$\frac{1}{R_p} = \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{3} + \frac{1}{6} = \frac{3}{6} = \frac{1}{2}$$
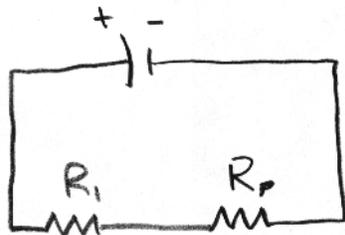
$$\frac{1}{R_p} = \frac{1}{2} \quad \underline{R_p = 2\Omega}$$



- Now, find the R_{eq} of them in series.

$$R_{eq} = R_1 + R_p = 4 + 2$$

$$\boxed{R_{eq} = 6\Omega}$$

← This is for the total circuit


b) Find the total current.

$$R_{eq} = 6\Omega \quad \Delta V = 12V$$

Ohm's Law

$$I = \frac{\Delta V}{R} = \frac{12V}{6\Omega} = \boxed{2A}$$

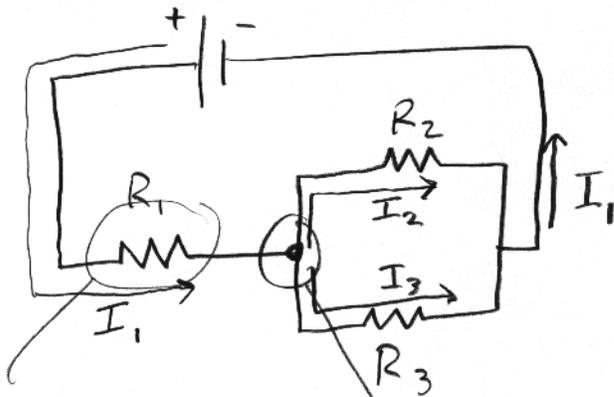c) Find the current flowing through each resistor.





Total current must pass through R_1

$$\boxed{I_1 = 2A}$$

Current splits at the junction (need ohm's law)


$$I_2 = \frac{\Delta V}{R_2} \leftarrow \text{we need the voltage}$$

ΔV - the drop can only be found with R_p

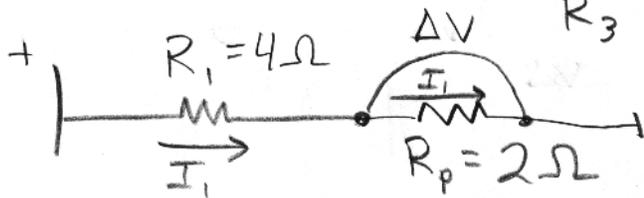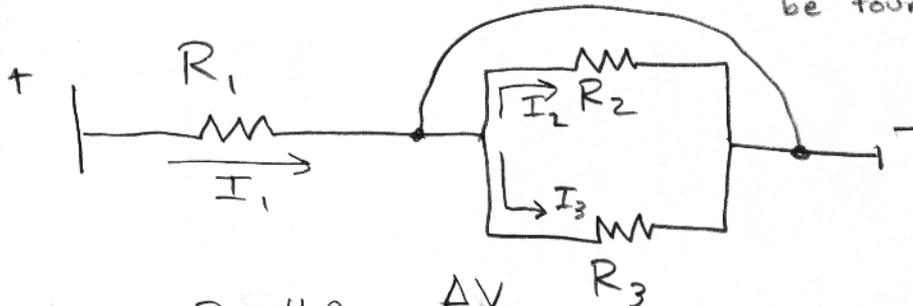

Since the current through is now just I_1
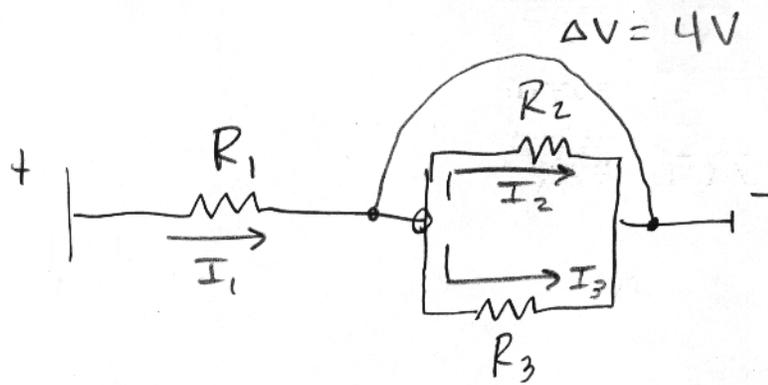
$$\Delta V = I_1 R_p = 2A \cdot 2\Omega = 4V$$



Resistors in parallel share potential difference

$$I_2 = \frac{\Delta V}{R_2} = \frac{4V}{3\Omega} = \boxed{1.33A}$$

For I_3 we could use $I_3 = \frac{\Delta V}{R_3} = \frac{4V}{6\Omega} = \boxed{0.66A}$


★ or we could use the junction rule

$$I_1 = I_2 + I_3$$

$$I_3 = I_1 - I_2 = 2A - 1.33A = \boxed{0.66A}$$


• The Junction Rule states that the current going into a junction will equal the current coming out.

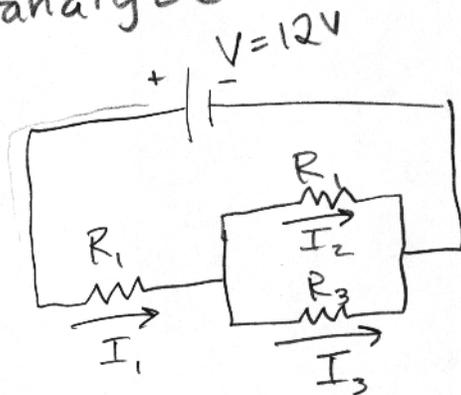Finally, lets analyze the entire situation,




Kirchhoff's loop rule will help us check our work.

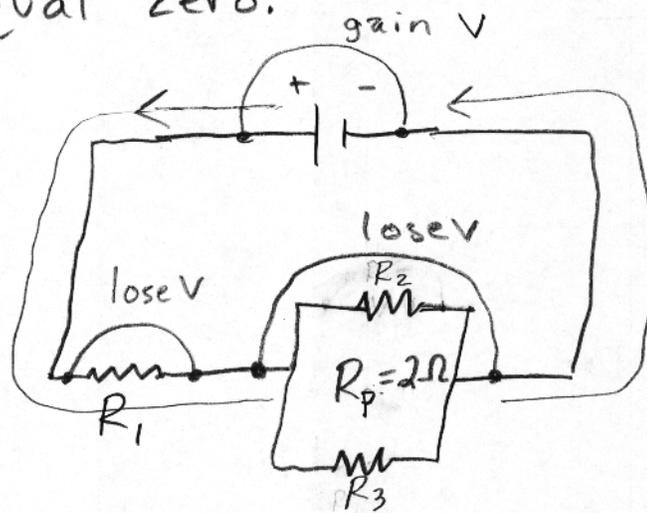- It states that the sum of potential drops and gains around any circuit loop will equal zero.



Ohm's Law
 $\Delta V = IR$

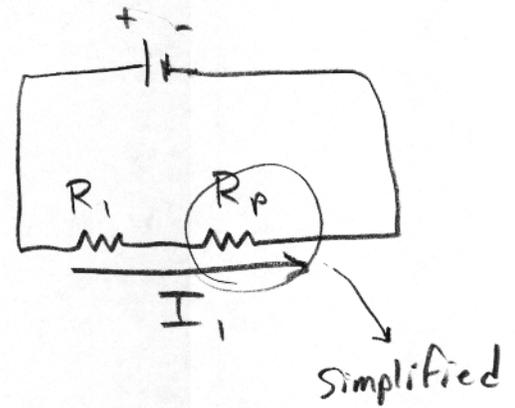

$$V - I_1 R_1 - I_1 R_p = 0$$

$$12V - (2A \cdot 4\Omega) - (2A \cdot 2\Omega) = 0$$

$$12 - 8 - 4 = 0$$

✓ Nice

