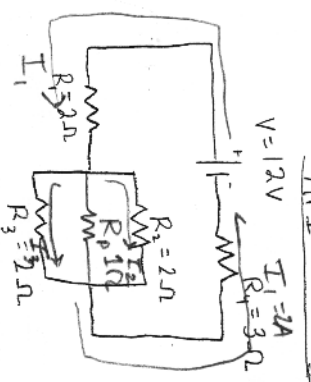


AP1 Circuit Practice

1)



$R_{eq} = 6\Omega$
 $I = \frac{\Delta V}{R_{eq}} = \frac{12}{6} = 2A$


- a) What is the current through each resistor?
 $I_1 = 2A$ (R_1)
 $I_2 = 1A$ (R_2)
 $I_3 = 1A$ (R_3)

- b) What is the power dissipated in each resistor?
 $P_1 = I_1^2 R_1 = 8W$
 $P_2 = I_2^2 R_2 = 2W$
 $P_3 = I_3^2 R_3 = 2W$
 $P_4 = I_4^2 R_4 = 12W$

- c) What is the power the battery supplies? Explain.
 $P = I_1 \Delta V = 24W$

Notice the power input equals output

2)

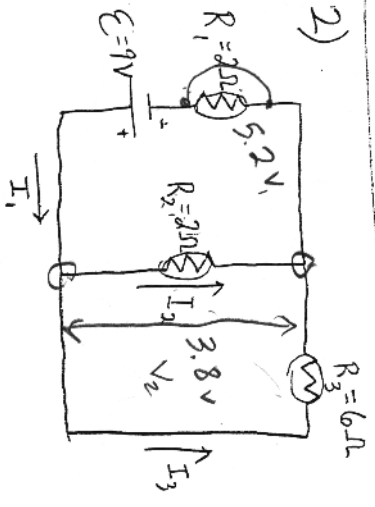

- a) Find each current.
 $I_1 = \frac{\Delta V}{R_{eq}} = \frac{9V}{3.5\Omega} = 2.6A$
 $I_2 = \frac{V_2}{R_2} = \frac{3.8}{2} = 1.9A$
 $I_3 = I_1 - I_2 = 0.7A$
- b) If the resistors are lightbulbs, rank them in order from brightest to dimmest.

Power = brightness

$P_1 = I_1^2 R_1 = 13.52W$

$P_2 = I_2^2 R_2 = 7.22W$

$P_3 = I_3^2 R_3 = 2.94W$


R_1, R_2, R_3

Req = 7Ω



$\frac{3}{2} \Omega + 2\Omega = \frac{7}{2} \Omega$

3)

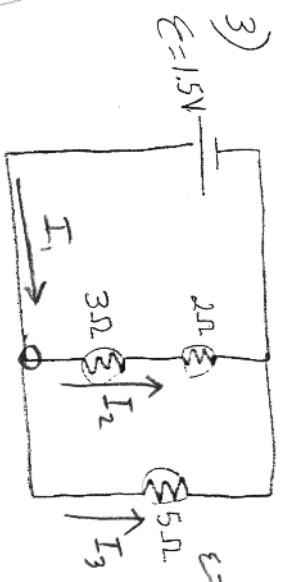



- a) Find the potential drop across the 2Ω resistor.
 $I_2 = 0.3A$
 $V = I_2 2\Omega = 0.6V$

- b) If the 2Ω resistor burns out, what is the current in the 5Ω resistor? Why did it go down?


- c) What would be the effect on the remaining lightbulbs? (3Ω, 5Ω after 2Ω burns out)

- d) What would be the advantage of wiring circuits in parallel? If one bulb goes out, the others on different paths can stay on.

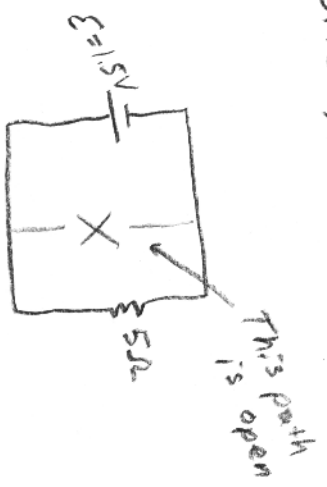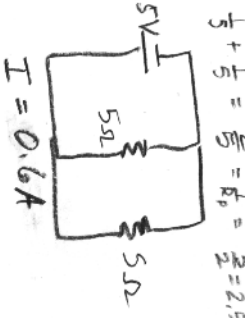- e) What would be a disadvantage of wiring in parallel? It uses more current, and more energy.



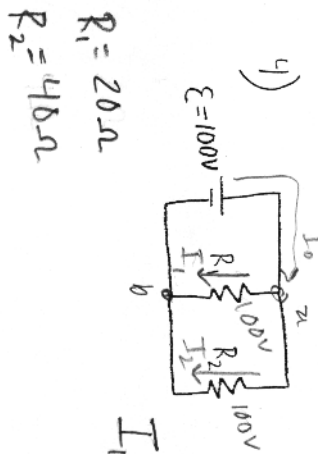$\frac{1}{5} + \frac{1}{5} = \frac{2}{5} = R_p = \frac{5}{2} = 2.5\Omega$





$R_1 = 20\Omega$
 $R_2 = 40\Omega$

1) How much energy is dissipated in each resistor over 1min?
 $I_1 = \frac{V}{R_1} = 5A$
 $I_2 = \frac{V}{R_2} = 2.5A$

2) Redraw the circuit with $E = P \cdot t$ the resistors in series. What is the effect on the power of the resistors?
 R_1 uses 30,000J per min
 R_2 uses 15,000J per min

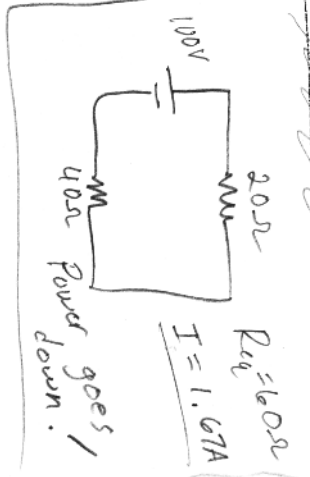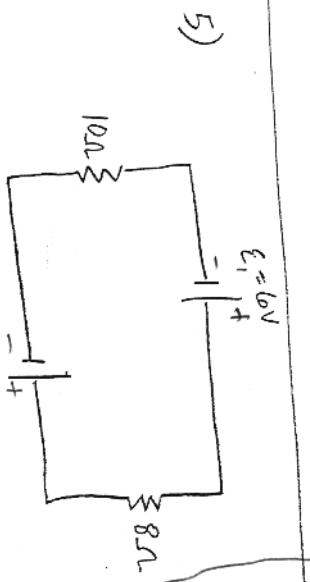
3) $P_1 = I_1^2 R_1 = 500W$
 $P_2 = I_2^2 R_2 = 250W$

$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{20} + \frac{1}{40}$
 $R_{eq} = 13.3\Omega$
 $I_0 = \frac{E}{R_{eq}} = \frac{100V}{13.3} = 7.52A$



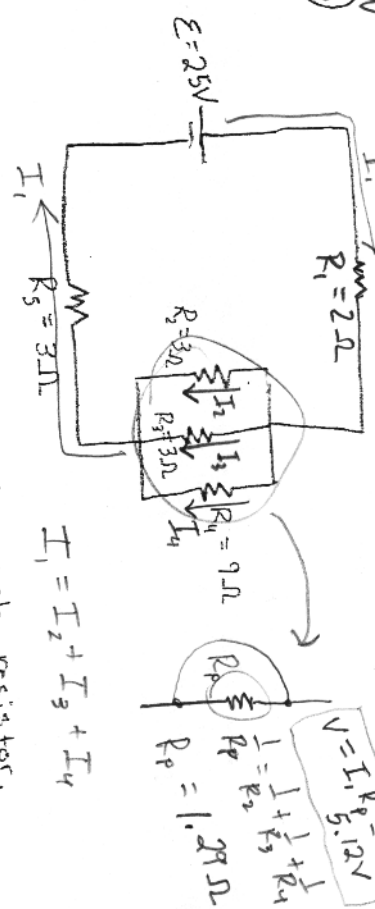a) Find the current in the circuit.
 $\mathcal{E}_2 - \mathcal{E}_1 = 6V$
 $R_{eq} = R_1 + R_2 = 18\Omega$

$I = \frac{\mathcal{E}_{tot}}{R_{eq}} = \frac{6V}{18\Omega} = 0.333A$



2) Find the current through each resistor.
 $R_{eq} = R_1 + R_p + R_5 = 6.29\Omega$
 $I_1 = \frac{E}{R_{eq}} = \frac{25V}{6.29\Omega} = 3.97A$ (R_1, R_5)
 $I_1 = I_2 + I_3 + I_4$

$I_2 = \frac{V}{R_2} = \frac{5.12V}{3\Omega} = 1.71A$
 $I_3 = \frac{V}{R_3} = \frac{5.12V}{3\Omega} = 1.71A$
 $I_4 = \frac{V}{R_4} = \frac{5.12V}{9\Omega} = 0.57A$

b) Find the power dissipated by each resistor.
 $P_1 = I_1^2 R_1 = 31.5W$
 $P_2 = I_2^2 R_2 = 2.77W$
 $P_3 = I_3^2 R_3 = 8.77W$
 $P_4 = I_4^2 R_4 = 2.92W$
 $P_5 = I_5^2 R_5 = 47.28W$

c) How much power does the battery supply?
 $P = I_b \mathcal{E} = 99.25W$

Sum of resistors power loss!